

Computer Architecture project

4-bit ALU Design & Implementation

Project Members:-

1. Ahmed Sayed Ahmed (8)
2. Ahmed Alaa Elden Yousef (13)
3. Hosny Mohamad Salem (42)
4. Shehata Abd ALmohsen (50)

Supervision of:-

Prof. Dr: Khaled El-Shafeay.

-

Objective:

Implementing a 4-bit ALU that performs the following functions:

1. Add.
2. Subtract.
3. Increment.
4. Decrement.
5. Transfer.
6. Bitwise AND.
7. Bitwise OR.
8. Bitwise XOR.
9. Bitwise NOT.

-

Features:

- The ALU has 2 input operands A and B, 4 bit each (in Operations such as Increment, Decrement, Transfer, Bitwise Not, Operand B is neglected, and the operation will be Performed on Operand A)
- It has 4 input pins (S2, S1, S0, Cin) to select the operation that will be performed by the ALU.
- S2 determines whether the operation to be performed is Arithmetic or Logic Operation. 0 for Arithmetic, 1 for Logic. ○ If S2 is 1, Cin will be neglected.
- The output consists of 4 bits (G3, G2, G1, G0) in addition to the Carry out pin (Cout).
- 3 Flags are included in the design:
 1. Z (Zero Flag) is set if the output of an arithmetic or logic operation is zero.
 2. V (Overflow Flag) is set when overflow occurs within an arithmetic operation is performed.
 3. N (Negative Flag) is set if the output of an arithmetic operation is negative.

• Tools:

The implementation and simulated on Protues.

Function Table:

- If $S_2 = 0$, the ALU performs Arithmetic operation according to the following table:


□ **TABLE 1**
Function Table for Arithmetic Circuit

Select		Input	$G = (A \mid Y \mid C_{in})$	
S_1	S_0	Y	$C_{in} = 0$	$C_{in} = 1$
0	0	all 0s	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	B	$G = A + B$ (add)	$G = A + B + 1$
1	0	\bar{B}	$G = A + \bar{B}$	$G = A + \bar{B} + 1$ (subtract)
1	1	all 1s	$G = A - 1$ (decrement)	$G = A$ (transfer)


- If $S_2 = 1$, the ALU performs Logical operation according to the following table:

S_1 S_0	Output	Operation
0 0	$G = A \wedge B$	AND
0 1	$G = A \vee B$	OR
1 0	$G = A \oplus B$	XOR
1 1	$G = \overline{A}$	NOT


(b) Function table

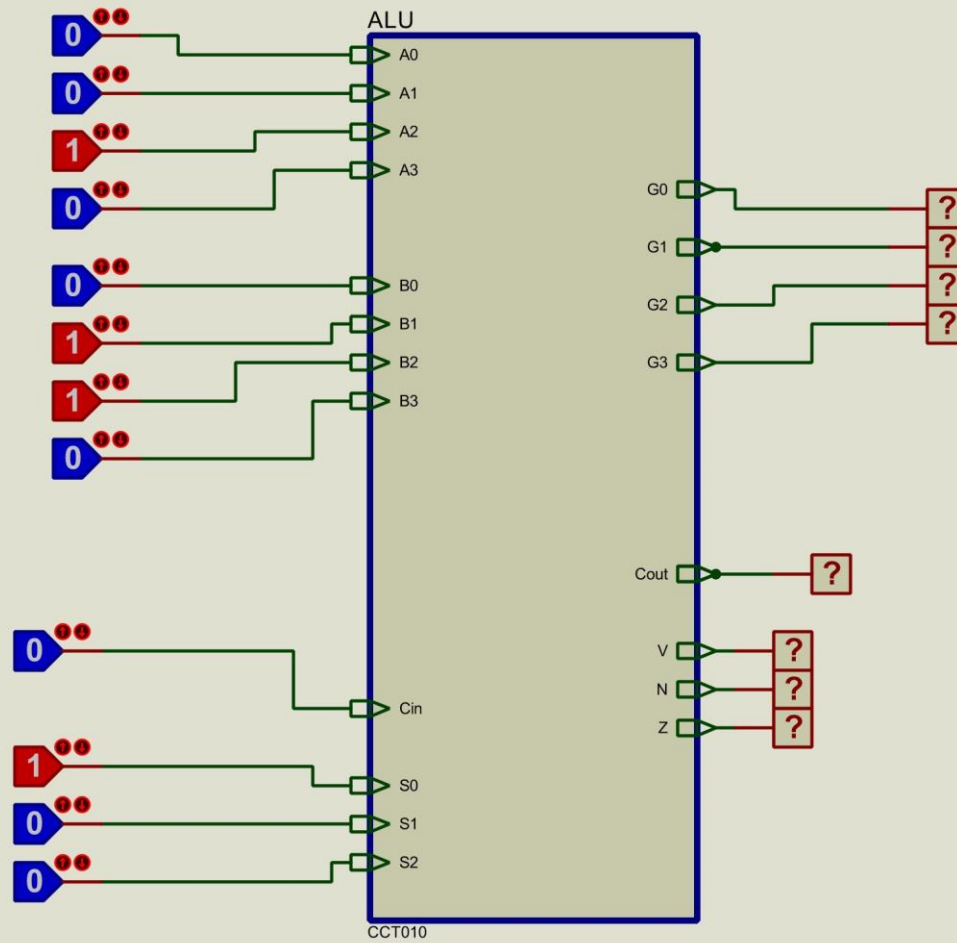


Logic Diagram of the 4bit ALU

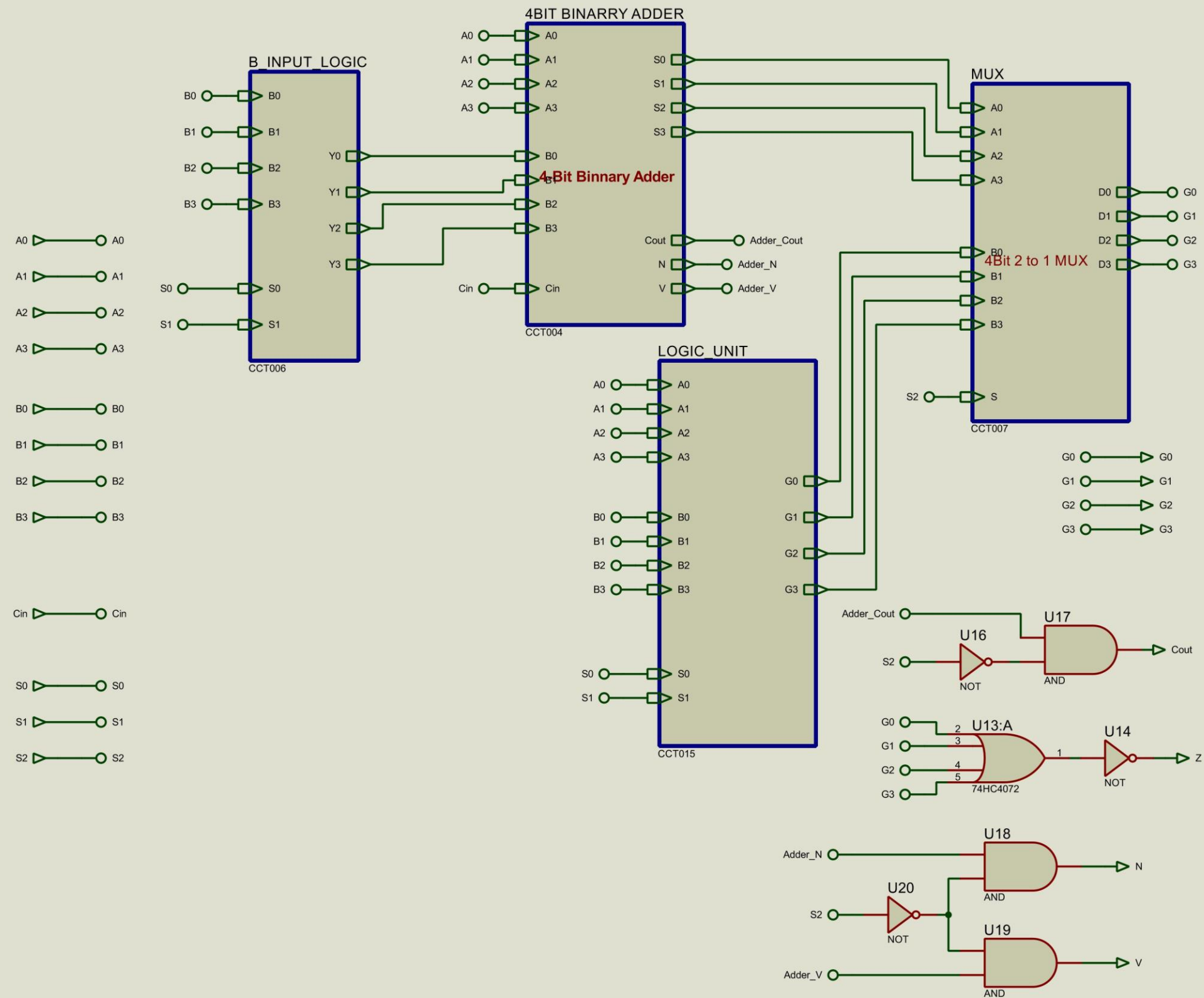

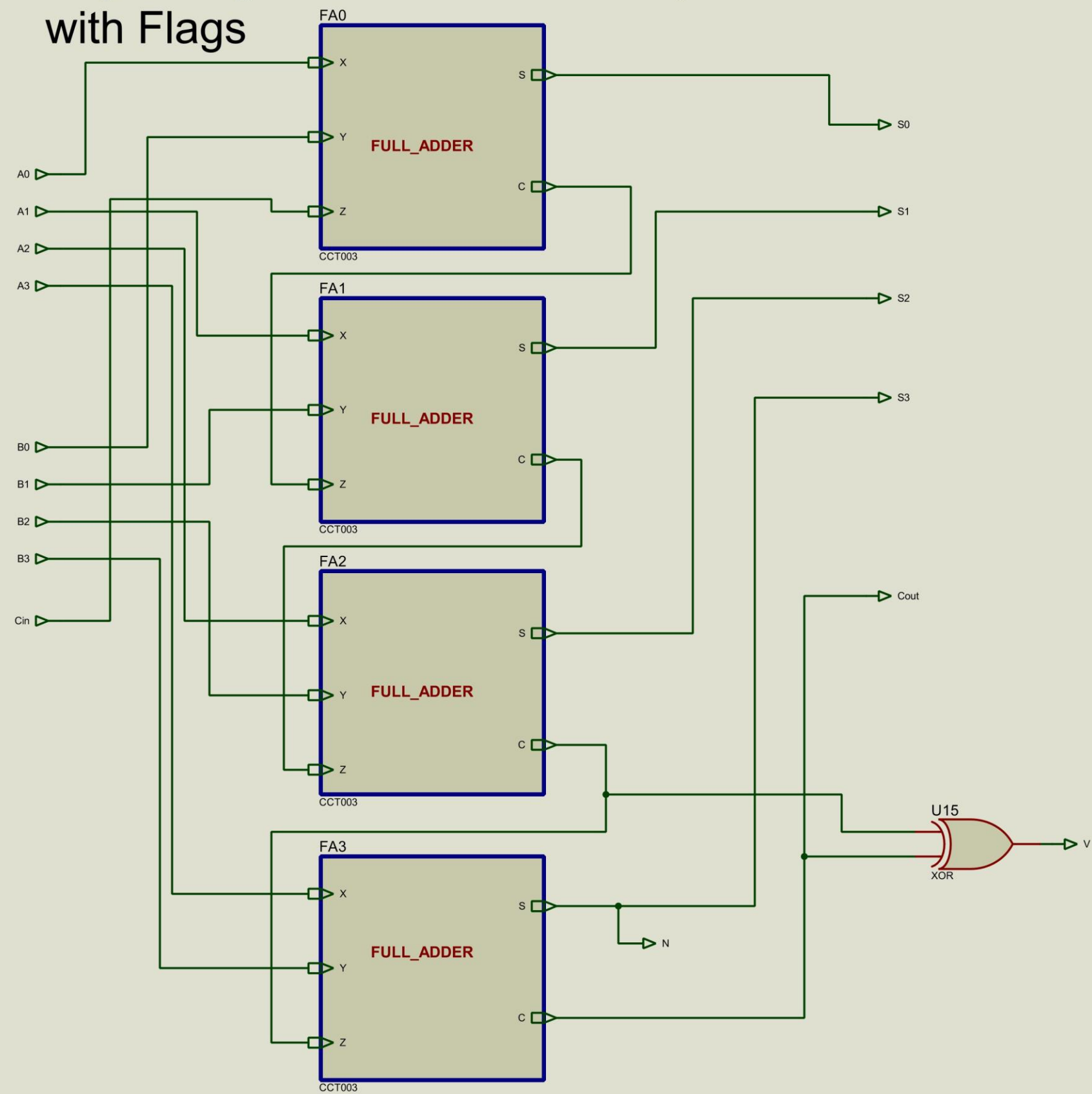
Logic Diagram of the 4bit Binary Adder with Flags




Design of the FULL ADDER

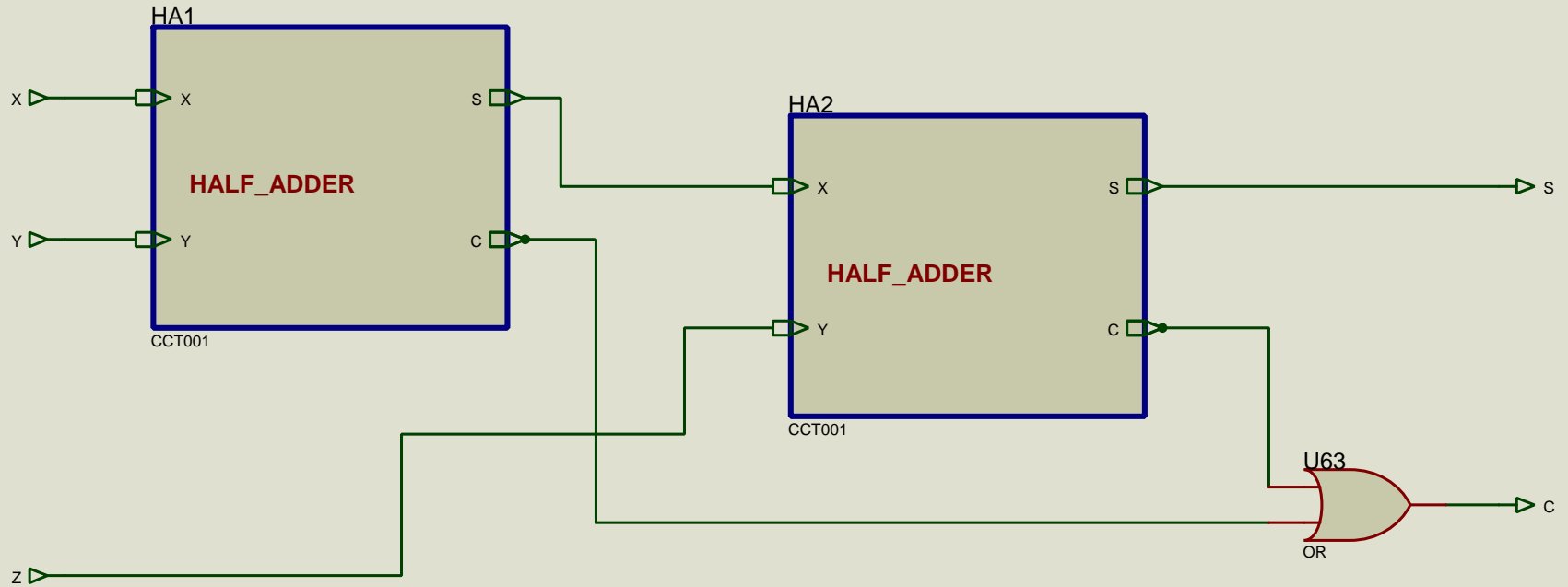


Design of the HALF ADDER






 


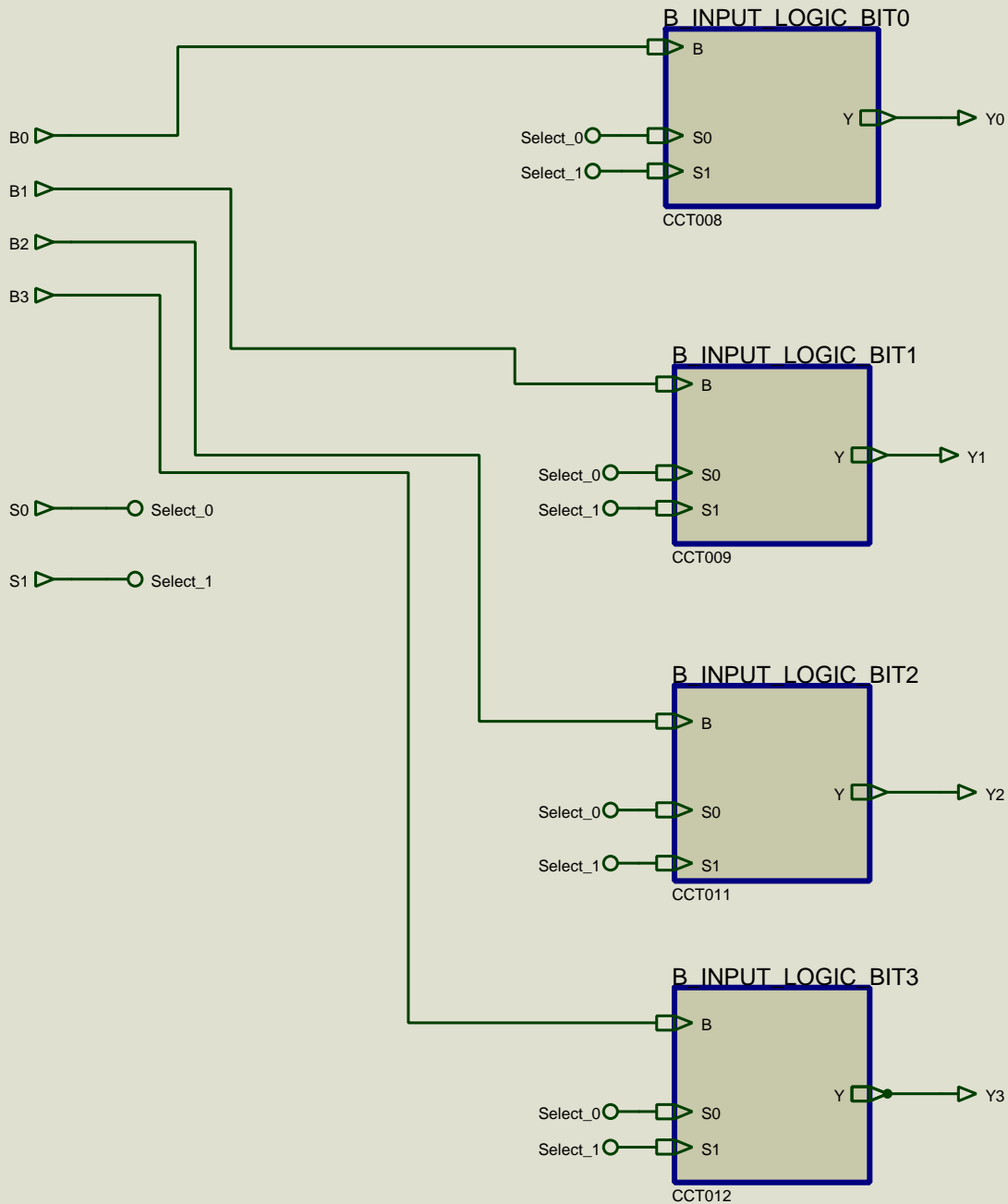

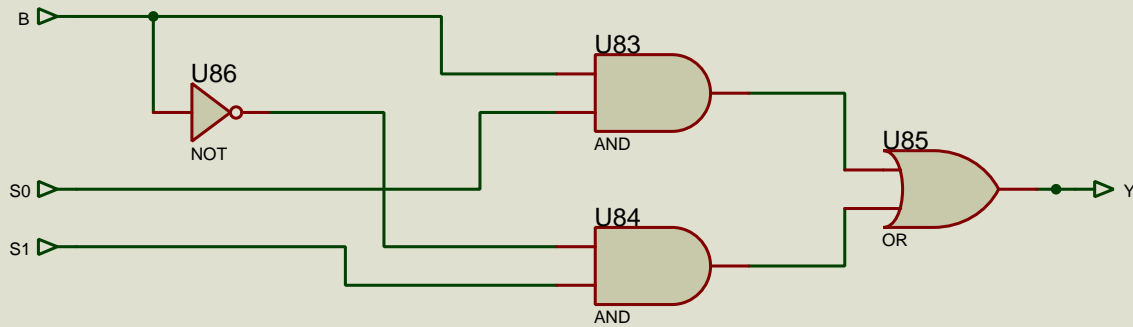
Logic Diagram of
the 4bit
Combinational
circuit that applied
on operand B



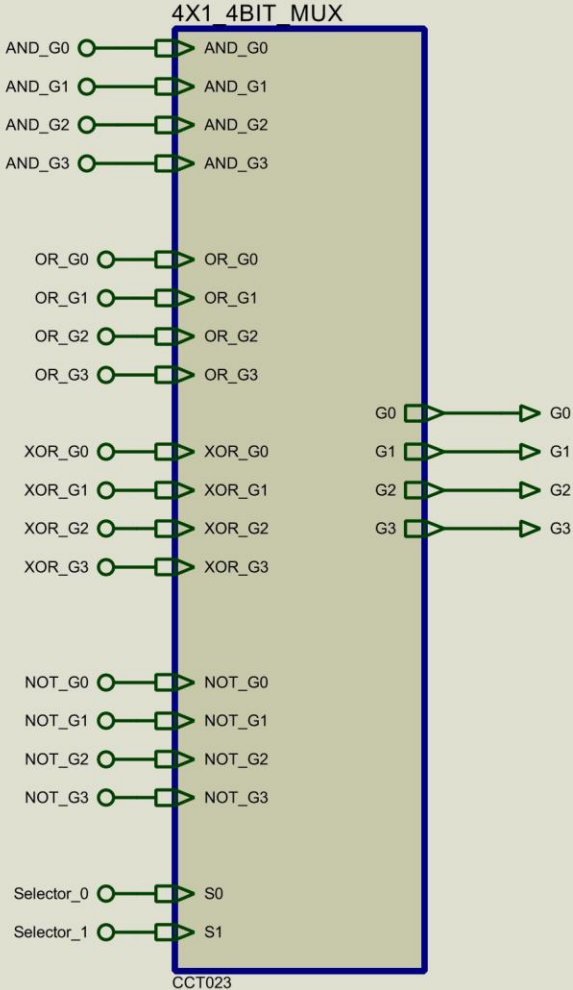  
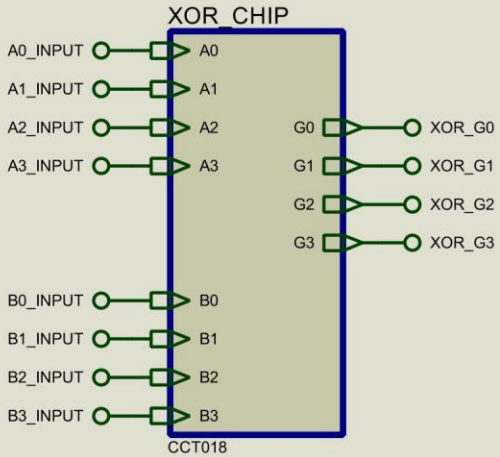
 
 
Design of Each bit of the combinational circuit that is applied on Operand B




Design of the Logic Unit

 





Design of the 4-bit AND Function

    


Design of the 4-bit OR Function

 


Design of the 4-bit XOR Function

 
 
 
 


Design of the 4-bit NOT Function

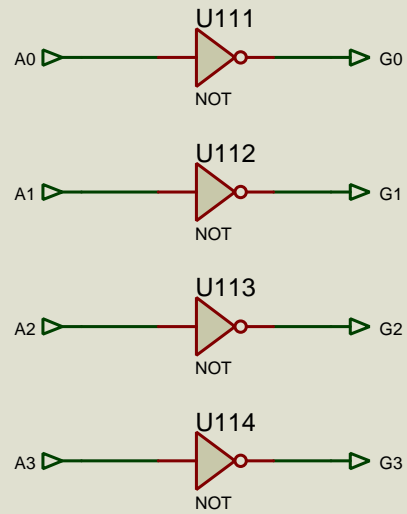

Design of the 4-bit 4 to 1 MUX

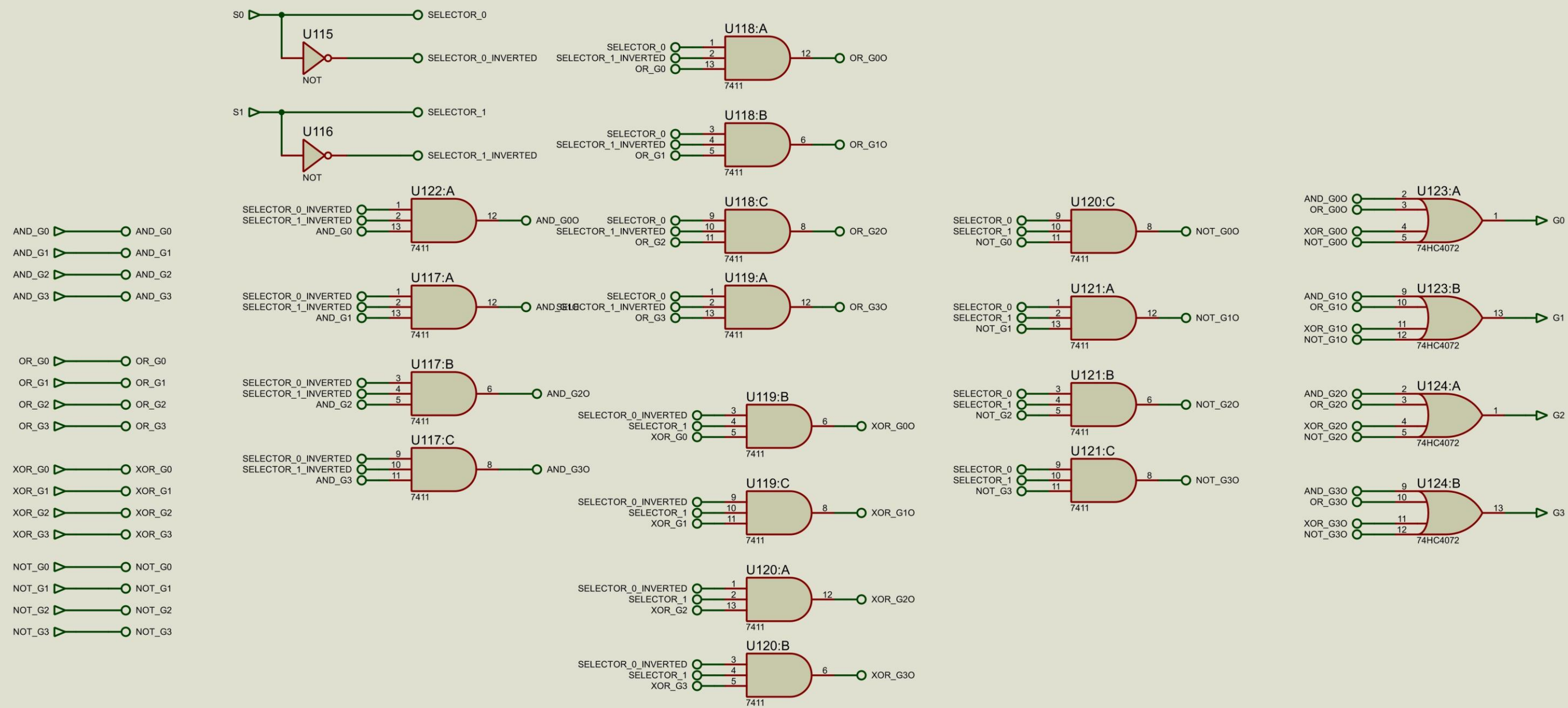

    

Internal design
of the 4-bit 2 to
1 MUX

Design of 1-bit 2 to 1 MUX

